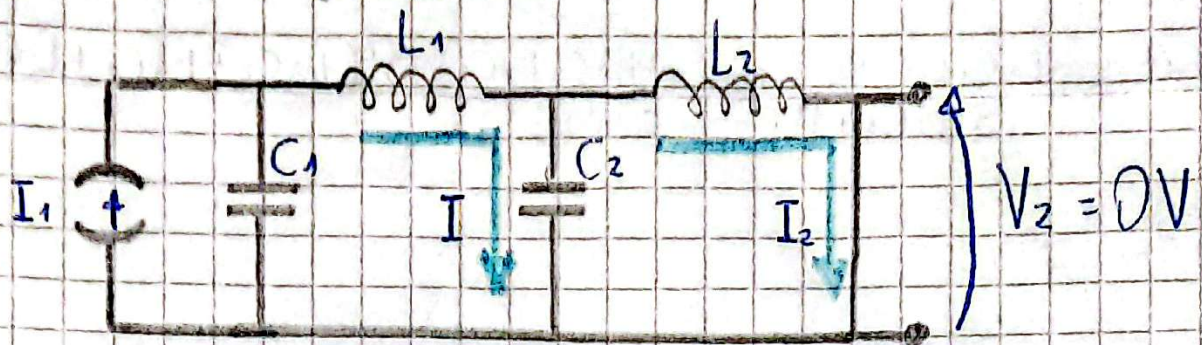


Verificación ejercicio 3



$$C_1 = 1 \text{ F} \quad ; \quad L_1 = 1/6 \text{ H}$$

$$C_2 = 12/5 \text{ F} \quad ; \quad L_2 = 5/18 \text{ H}$$

Por mallas:

$$I \cdot \left(\frac{1}{5} + \frac{1}{6} \cdot 5 + \frac{5}{12 \cdot 5} \right) - \frac{I_1}{5} - \frac{5}{12 \cdot 5} \cdot I_2 = 0 \quad (A)$$

$$I_2 \left(\frac{5}{12 \cdot 5} + \frac{5 \cdot 5}{18} \right) - \frac{5}{12 \cdot 5} \cdot I = 0 \rightarrow I = I_2 \left(1 + \frac{2}{3} \cdot 5^2 \right) \quad (B)$$

Reemplazo (B) en (A):

$$I_2 \left(1 + \frac{2}{3} \cdot 5^2 \right) \left(\frac{17 + 25^2}{12 \cdot 5} \right) - \frac{I_1}{5} - \frac{5}{12 \cdot 5} \cdot I_2 = 0$$

$$I_2 \left(\frac{17 + 25^2}{12 \cdot 5} + \frac{(34/3) \cdot 5^2 + (4/3) \cdot 5^4}{12 \cdot 5} - \frac{5}{12 \cdot 5} \right) = \frac{I_1}{5}$$

$$I_2 \left(\frac{5^4 + 10 \cdot 5^2 + 9}{12 \cdot 5} \right) = \frac{3}{4} \cdot \frac{I_1}{5}$$

$$\frac{I_2}{I_1} = \frac{9}{(5^2 + 9)(5^2 + 1)}$$