
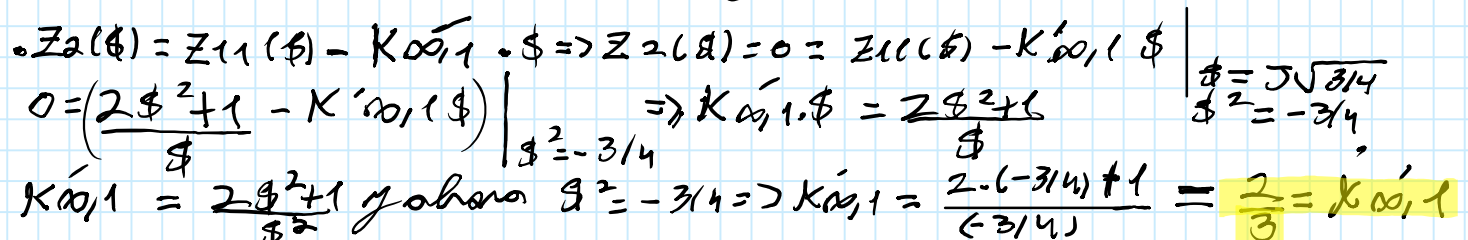


sábado, 6 de septiembre de 2025 09:38

$$\frac{V_2}{V_1} = \frac{s^2 + 1}{2s^2 + 1}$$

- $$T(\beta) = \frac{V_2}{V_1} = \frac{\beta^2 + 1}{2\beta^2 + 1} = \frac{Z_{21}}{Z_{11}} \rightarrow \text{Transparencia}$$

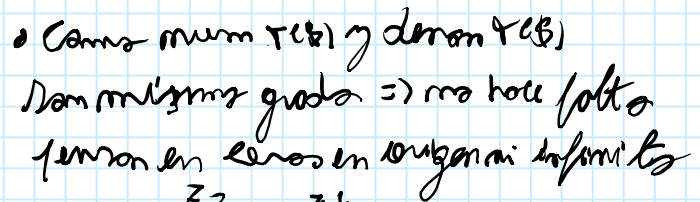- ## (10) Métodos gráficos de síntesis y generación



$$K_{0,1} = \frac{2g^2+1}{g^2} \text{ ahora } g^2 = -3/4 \Rightarrow K_{0,1} = \frac{2 \cdot (-3/4) + 1}{(-3/4)} = \frac{2}{3} = K_{0,1}$$

Ejercicio 5 (a) - Hoja 2

sábado, 6 de septiembre de 2025 09:39

$$\bullet Z_2(s) = \frac{2s^2+1}{s} - (2/3) \cdot s = \frac{2s^2+1-(2/3)s^2}{s} = \frac{(4/3)s^2+1}{s} = Z_2(s)$$

$$\bullet Z_4(s) = Z_2(s) - K_{0,2} \cdot s, \quad Z_4(s) = 0 = (Z_2(s) - K_{0,2} \cdot s) \Big|_{s^2=-1}$$

$$\Rightarrow 0 = \frac{(4/3)s^2+1}{s} - K_{0,2} \cdot s \Rightarrow K_{0,2} \cdot s = \frac{(4/3)s^2+1}{s} \Big|_{s^2=-1}$$


$$K_{0,2} = \frac{(4/3) \cdot s^2+1}{s^2} \text{ y ahora } s^2 = -1 \Rightarrow \frac{(4/3)(-1)+1}{(-1)} = 1/3 = K_{0,2}$$

$$\bullet Z_4(s) = \frac{(4/3)s^2+1}{s} - (1/3)s = \frac{(4/3)s^2+1-(1/3)s^2}{s} = \frac{s^2+1}{s} = Z_4(s), \quad \frac{s}{s+1}$$

$$\bullet Y(s) = Y_4(s) - \frac{2K_3 \cdot s}{s^2+(\sqrt{1})^2}, \quad 2K_3 = \lim_{s^2 \rightarrow -1} \frac{Y_4(s)}{s} \cdot (s^2+(\sqrt{1})^2) = \lim_{s^2 \rightarrow -1} \frac{s}{s^2+1} \cdot \frac{s^2+1}{s} = 1$$

$$2K_3 = 1$$

3º Circuitos

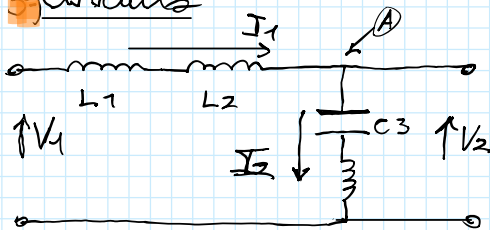

$$L1 = K_{0,1} = 2/3$$

$$L2 = K_{0,2} = 1/3$$

$$Y_{L3,C3} = \frac{1}{Z_{L3,C3}} = \frac{1}{sL3 + \frac{1}{C3 \cdot s}} = \frac{C3 \cdot s}{s^2 L3 C3 + 1} \quad \frac{1(C3 \cdot L3)}{1(C3 \cdot L3)} = \frac{(1/3) \cdot s}{s^2 + 1/3 \cdot C3}$$

$$Y_{L3,C3} = \frac{2K1 \cdot s}{s^2+(\sqrt{1})^2} \Rightarrow \begin{cases} 2K1 = 1/L3 \Rightarrow L3 = \frac{1}{2K1} = 1 = L3 \\ (\sqrt{1})^2 = \frac{1}{L3 \cdot C3}, \quad 1 = \frac{1}{1 \cdot C3} \Rightarrow C3 = 1 \end{cases}$$

4º Verificación

$$V_2 = V_1 \cdot \frac{Y_{L1,L2}}{Y_{L3,C3} + Y_{L1,L2}} \rightarrow \text{Divisor de tensión}$$

$$\frac{V_2}{V_1} = \frac{\frac{sL1 + sL2}{2K1s + \frac{1}{sL1 + sL2}}}{\frac{sL1 + sL2}{2K1s + \frac{1}{sL1 + sL2}} + \frac{s}{s^2 + 1}} = \frac{1}{2K1s(sL1 + sL2) + 1}$$

$$\frac{V_2}{V_1} = \frac{s^2 + 1}{s^2 2K1 \cdot (L1 + L2) + s^2 + 1} = \frac{s^2 + 1}{2s^2 + 1} = \frac{V_2(s)}{V_1(s)} \sqrt{s^2 + (\sqrt{1})^2}$$