


9) sintetizar en un circuito esquelero

$$\begin{aligned} T(8) &= \frac{(8^2+1)(8^2+4)}{(8^2+1)(8^2+3)} \\ &= \frac{(8^2+4)(8^2+6)}{3(8^2+2)} \\ &= \frac{(8^2+1)(8^2+3)}{3(8^2+2)} \end{aligned}$$



$$\Rightarrow T = \frac{V_2}{V_1} = \frac{Z_{21}}{Z_{11}} = -\frac{y_{21}}{y_{22}} \quad \left| \begin{array}{cccc} \times & \times & 0 & 0 \\ 1 & 5 & 2 & 3 \end{array} \right| \Rightarrow J_N$$

Tenemos que usar las funciones de excitación que se conocen como sintetizantes


Necesitamos los pesos de T

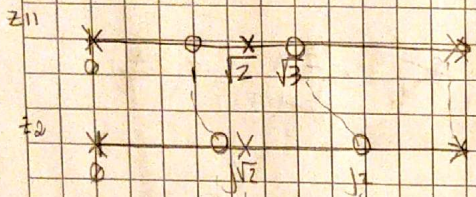


removemos
de forma
parcial

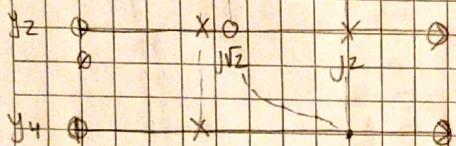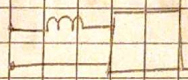

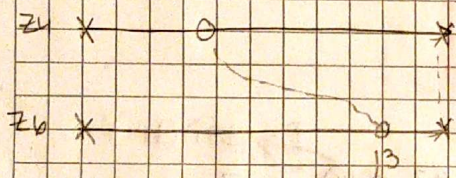
al remover un
pob finito, el
cso que llega deja
un alor reactivo



nuevamente
de forma
parcial

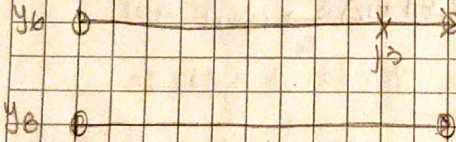

removernos el
pelo en
admiración

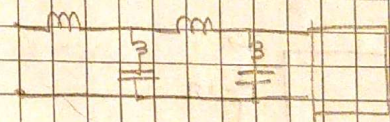

$$\Rightarrow z_2 - z_1 = K' \delta \quad \wedge \quad z_2 = z_1 + K' \delta = 0 \quad \Leftrightarrow \quad K' \delta = \frac{z_1}{\delta} = \frac{\frac{z_1}{\delta} + z_2}{\frac{z_1}{\delta} + z_2 + 1} = \frac{z_1}{z_1 + z_2 + 1}$$

$$Z_2 = \frac{(5^2+1)(5^2+6)}{5(5^2+2)} - \frac{2}{5} = \frac{5^4 + 5^2 + 30}{5(5^2+2)} = \frac{\cancel{5^4} + 5^2 + 30 - \cancel{5^4} - 2}{5(5^2+2)} = \frac{28}{5(5^2+2)}$$

$$\Rightarrow y_2 = \frac{1}{(b^2+4)} \Rightarrow y_4 = y_2 - \lim_{b^2+4 \rightarrow -4} \frac{1}{b^2+4} \cdot \frac{1}{(b^2+4)}$$

$$y_4 = \frac{3(8^2 + 2)}{\frac{5}{8}(8^2 + 2)(8^2 + 4)} - \frac{8}{8^2 + 4}$$

$$K = \lim_{q^2 \rightarrow -4} \frac{q^2 + 2}{q^2(q^2 + 5)} = \frac{1}{1} \cdot \frac{1}{-20}$$

$$= \frac{3(b^2+4)}{\frac{5}{6}(b^2+\frac{6}{5})(b^2+4)} = \frac{3 \cdot 2 \cdot 3}{\frac{5}{6}(b^2+\frac{6}{5})(b^2+4)} = \frac{36}{5(b^2+\frac{6}{5})(b^2+4)}$$

$$\Rightarrow Z_4 = \frac{\frac{2}{3}(s^2 + \frac{6}{5})(s^2 + 4)}{\frac{2}{3}s^2 + \frac{8}{5}s} = \frac{\frac{2}{3}(s^2 + \frac{6}{5})(s^2 + 4)}{\frac{2}{3}(s^2 + 4s)}$$

$$\Rightarrow Z_6 = Z_4 - K' \alpha s \quad \text{on } Z_4|_{s=-1} - K' \alpha s = 0 \Rightarrow Z_4|_{s^2=-9} = K' \alpha s$$


$$\text{on } K' \alpha = \frac{Z_4|_{s^2=-9}}{s|_{s^2=-9}} = \frac{\frac{2}{3}(s^2 + \frac{6}{5})(s^2 + 4)}{\frac{2}{3}s(s^2 + 4)} \cdot \frac{1}{s|_{s^2=-9}} = \frac{\frac{2}{3}(-9 + \frac{6}{5})}{\frac{2}{3}(-9)} = \frac{\frac{2}{3}(-9 + \frac{6}{5})}{\frac{2}{3}(-9)} = \frac{91}{48}$$



$$Z_6 = \frac{\frac{2}{3}(s^2 + \frac{6}{5})}{\frac{2}{3}s} - \frac{91}{48} \cdot \frac{1}{s} = \frac{\frac{2}{3}(s^2 + \frac{6}{5}) - \frac{91}{48}s \cdot \frac{2}{3}s}{\frac{2}{3}s} = \frac{\frac{1}{12}s^2 + \frac{2}{9}}{\frac{2}{3}s} = \frac{1}{12}(s^2 + 9)$$

$$\Rightarrow Y_6 = \frac{\frac{2}{3}s}{\frac{1}{12}(s^2 + 9)} \rightarrow Y_8 = Y_6 - \frac{Ks}{s^2 + 9} \quad \text{on } K = \lim_{s^2 \rightarrow -9} \frac{s^2 + 9}{s} \cdot \frac{\frac{2}{3}s}{\frac{1}{12}(s^2 + 9)} = \frac{24}{7}$$
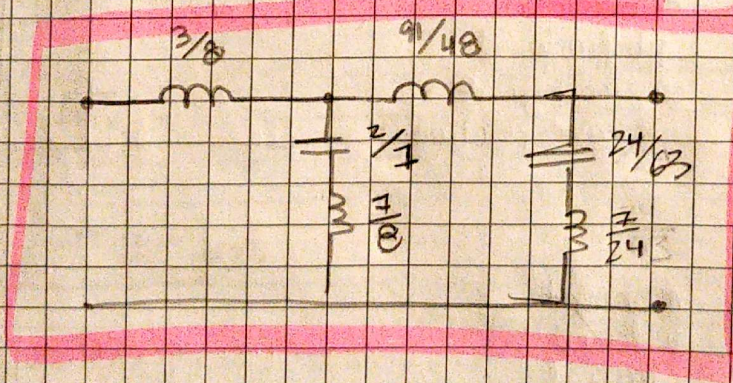
$$Y_8 = \frac{\frac{2}{3}s}{\frac{1}{12}(s^2 + 9)} - \frac{\frac{24}{7}s}{(s^2 + 9)} = \frac{\frac{2}{3}s - \frac{24}{7}s \cdot \frac{1}{12}}{\frac{1}{12}(s^2 + 9)} = 0$$



8)

Sin te tizer (quadro) RC con

-T-

11 47

→ (s+1)(s+4)