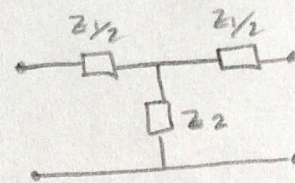


7) $f_c = 1K$ con 600Ω , $f_{att} \infty$ en $1,05K$, secciones de $m=0,6$ IN y OUT.

- $f_c = 1KHz \Rightarrow \omega_c = 2\pi f_c = 2000\pi$
- $f_0 = 1K05Hz \Rightarrow \omega_0 = 2\pi f_0 = 2100\pi$



una red T prueba.

$$Z_1 = jL$$

$$Z_2 = \frac{1}{jC}$$

$$R_0 = \sqrt{\frac{L}{C}} = (600\Omega) \quad (I)$$

$$Z_{OT} = \sqrt{\frac{L}{C}} \sqrt{1 - \frac{\omega^2 LC}{4}}$$

(corte donde $Z_{OT} = 0$)

$$1 - \frac{\omega_c^2 LC}{4} = 0$$

$$1 = \frac{\omega_c^2 LC}{4}$$

$$4 = \omega_c^2 LC$$

$$\omega_c = \sqrt{\frac{4}{LC}}$$


frec de corte

$$\omega_c = 2000\pi = \frac{2}{\sqrt{LC}}$$

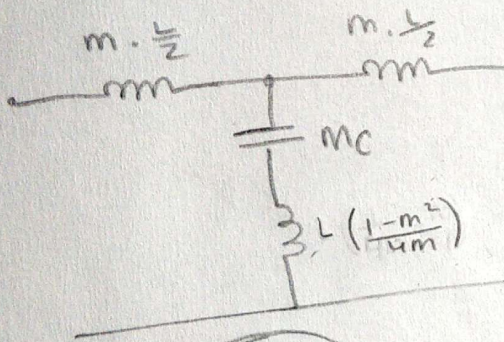(I) donde $L = C \cdot 360K$.


$$2000\pi = \frac{2}{\sqrt{C \cdot 360K \cdot C}}$$

$$\Rightarrow C = 530,5nF \Rightarrow L = 190,9mH$$



ELLO

$m=0,6$

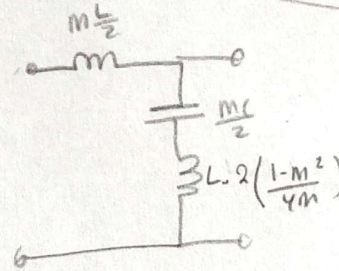

HERMISECCION

$$\frac{m \cdot L}{2} = 57,27mH$$

$$\frac{mC}{2} = 159,15nF$$

$$L \cdot 2 \left(\frac{1-m^2}{4m} \right) = 101,86mH$$

$$\omega_{00} = \frac{\omega_c}{\sqrt{1-m^2}} = 2500\pi \neq 2000\pi$$

tenge que derivar

$$m = \sqrt{1 - \left(\frac{f_c}{f_0} \right)^2} = 0,305$$

$$\frac{m \cdot L}{2} = 29,11mH$$

$$m \cdot C = 161,8nF$$

$$L \left(\frac{1-m^2}{4m} \right) = 141,92mH$$

