

Ej. 10) $W_c = 20\text{ K mod } 1A$


$R_L = 600\ \Omega$

$W_1 = 22\text{ K}$


$W_2 = 40\text{ K}$

Unión Celosa T.

NOTA

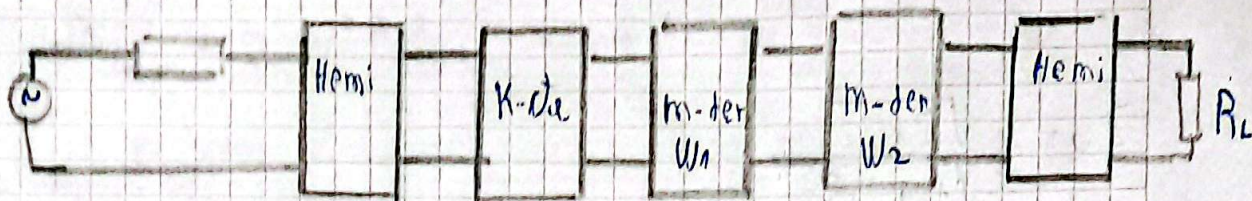


Plantear celda K-de:

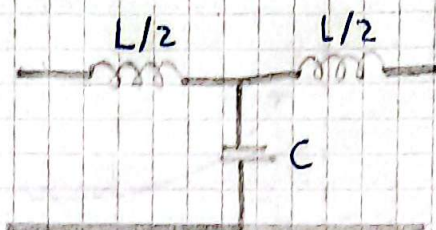

$$R_0 = \sqrt{\frac{L}{C}}$$

$$W_c = \frac{2}{\sqrt{LC}} \longrightarrow C = 166,6 \text{ nF}$$


$$L = 60 \text{ mH}$$

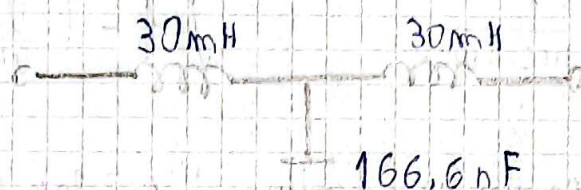

Calcular m para $W_\infty = W_1$:

$$W_1 = 22 \text{ K rad/s}$$
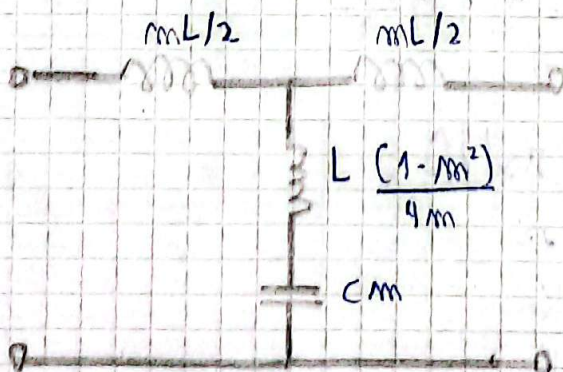
$$W_1 = \frac{W_c}{\sqrt{1-m^2}} \longrightarrow m = 0,417$$




En $W_\infty = W_2$:


$$W_2 = 40 \text{ K rad/seg}$$

$$W_2 = \frac{W_c}{\sqrt{1-m^2}} \longrightarrow m = 0,866$$


En la hemi-rección:

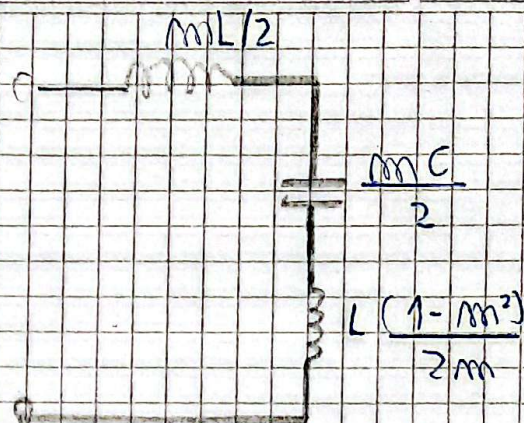

$$W_{\infty} \Big|_{m=0,6} = 25 \text{ K} \frac{\text{rad}}{\text{s}}$$

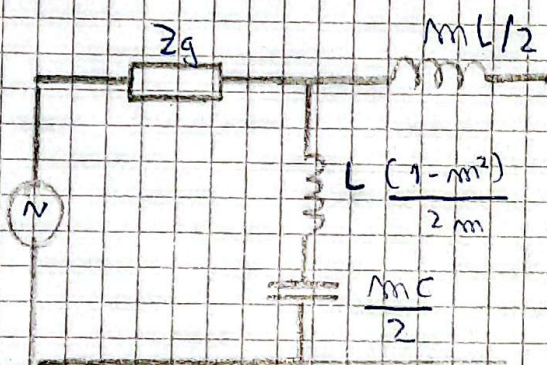

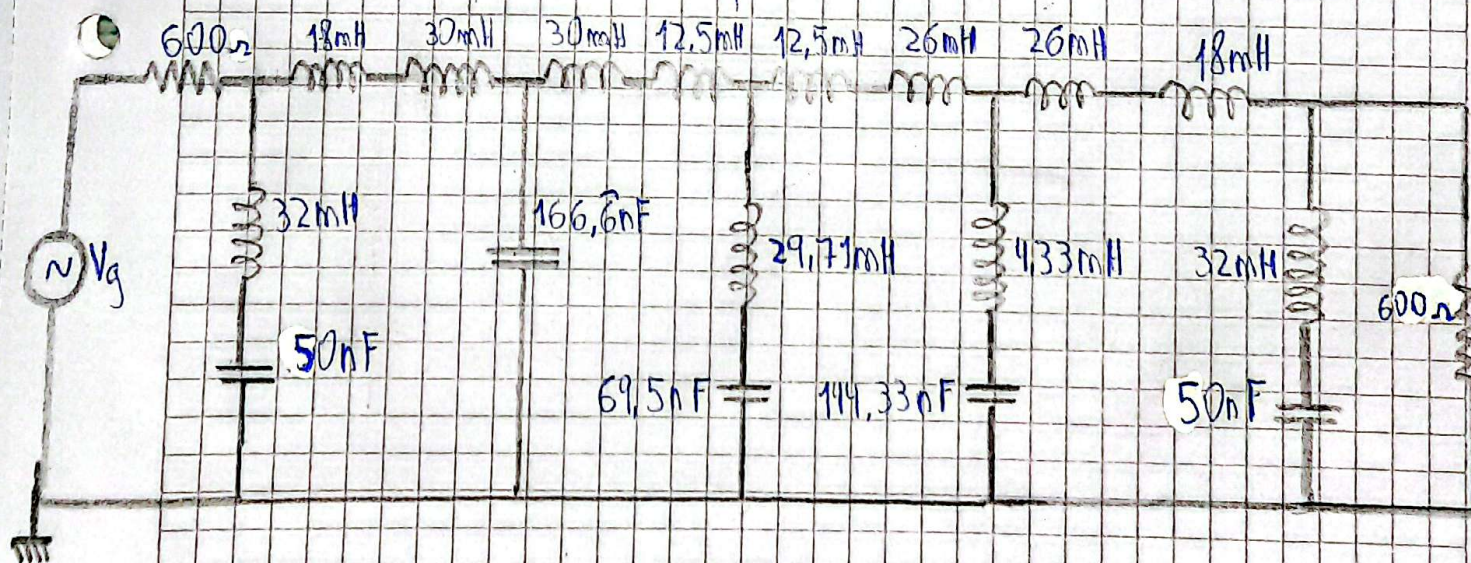Finalmente, el circuito completo se vería así:



NOTA