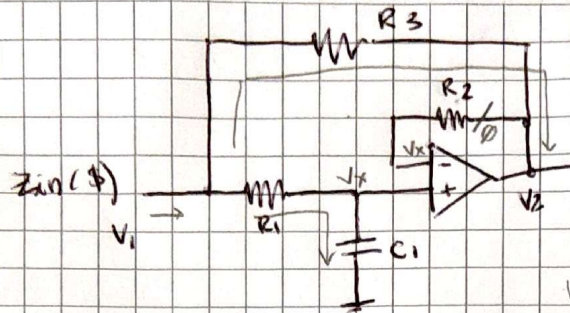


2b)



$$\rightarrow \frac{V_{in} - V_x}{R_1} = \frac{V_x - 0}{\frac{1}{sC_1}}$$

$$\rightarrow \frac{V_o - V_x}{R_2} = 0 \quad \left\{ \begin{array}{l} V_o = V_x \end{array} \right.$$

$$\rightarrow I_{in} = \frac{V_i - V_x}{R_1} + \frac{V_i - V_o}{R_3}$$

$$I_{in} = \frac{V_i - V_o}{R_1} + \frac{V_i - V_o}{R_3}$$

$$I_{in} = V_i \left(\frac{1}{R_1} + \frac{1}{R_3} \right) - V_o \left(\frac{1}{R_1} + \frac{1}{R_3} \right)$$

$$I_{in} = V_i \frac{R_3 + R_1}{R_1 R_3} - V_o \frac{R_3 + R_1}{R_3 R_1}$$

$$I_{in} = \frac{V_i (R_3 + R_1)}{R_1 R_3} \left(1 - \frac{1}{sC_1 R_1 + 1} \right) = \frac{V_i (R_3 + R_1)}{R_1 R_3} \frac{sC_1 R_1 + 1 - 1}{sC_1 R_1 + 1}$$

$$I_{in} = V_i \frac{(R_3 + R_1) \cdot sC_1 R_1}{(sC_1 R_1 + 1) R_1 R_3} = V_i \frac{sC_1 R_1 (R_3 + R_1)}{(sC_1 R_1 + 1) R_1 R_3}$$

$$\frac{V_{in}}{I_{in}} = Z_{in} = \frac{(sC_1 R_1 + 1) R_3}{sC_1 R_1 (R_3 + R_1)} = \frac{sC_1 R_1 R_3 + R_3}{s(C_1 R_1 + C_1 R_3)} = \frac{C_1 R_1 R_3}{C_1 R_1 + C_1 R_3} + \frac{R_3}{s(C_1 R_1 + C_1 R_3)}$$

$$\frac{V_{in} - V_o}{R_1} = V_o sC_1$$

$$V_{in} - V_o = V_o sC_1 R_1$$

$$V_{in} = V_o (sC_1 R_1 + 1)$$

$$V_o = \frac{V_{in}}{sC_1 R_1 + 1}$$