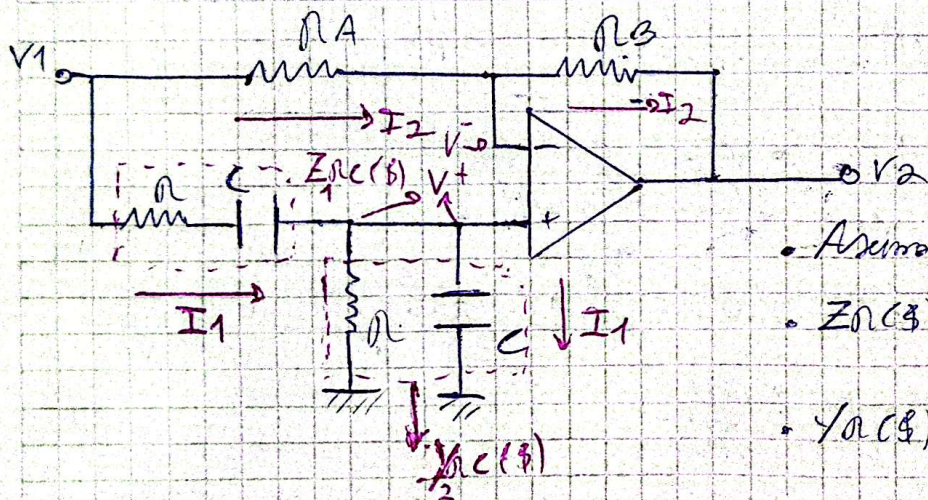


Ejercicio 4)

b)

- Filtro Paso Todo o Notador de Fosa, $g_{num}(s) = \frac{V_2(s)}{V_1(s)}$ tanto el módulo, la fase, y el diagrama de polos y ceros
- Toma $\frac{R_2}{R_1} = 1$ y $\frac{R_A}{R_B} = 5$



- Asumo filtro ideal
- $Z_R(s) = R$, $Z_C(s) = \frac{1}{sC}$
- $Y_R(s) = \frac{1}{R}$, $Y_C(s) = sC$
- $V^+ = V^-$ por configuración aislada

$$V^+ = V^- = V_1(s) \frac{Y_{RC}(s)}{Y_{RC}(s) + Y_{RA}(s)}, \quad I_{in}(s) = I_1(s) + I_2(s)$$

$$I_1(s) = (V_1(s) - V^+) \cdot Y_{RA}(s) = (V^+ - 0V) \cdot Y_{RC}(s) \rightarrow \text{Por igualdad de voltajes análogamente al ejercicio 4) } \Rightarrow \text{se obtiene}$$

$$V^+ = V_1(s) \frac{Y_{RC}(s)}{Y_{RC}(s) + Y_{RA}(s)} \quad \text{con } V^+ = V^-$$

$$I_2(s) = (V_1(s) - V^-) \cdot Y_{RA}(s) = (V^- - V_2(s)) \cdot Y_{RB}(s)$$

$$\Rightarrow V_1(s) \cdot Y_{RA}(s) - V^- \cdot Y_{RA}(s) = V^- \cdot Y_{RB}(s) - V_2(s) \cdot Y_{RB}(s)$$

$$\Rightarrow V_1(s) \cdot Y_{RA}(s) + V_2(s) \cdot Y_{RB}(s) = V^- \cdot Y_{RB}(s) + V^- \cdot Y_{RA}(s)$$

$$V_1(s) \cdot Y_{RA}(s) + V_2(s) \cdot Y_{RB}(s) = V^- \cdot (Y_{RB}(s) + Y_{RA}(s))$$

NOTA

$$V_1(\$) \cdot Y_{RA}(\$) + V_2(\$) \cdot Y_{RB}(\$) = V_1(\$) \cdot \frac{Y_{RC}(\$)}{Y_{RC}(\$) + \frac{1}{2}Y_{RB}(\$)} \cdot (Y_{RB}(\$) + Y_{RA}(\$))$$

$$V_2(\$) \cdot Y_{RB}(\$) = V_1(\$) \left(\frac{Y_{RC}(\$) \cdot Y_{RB}(\$)}{Y_{RC}(\$) + \frac{1}{2}Y_{RB}(\$)} + \frac{Y_{RC}(\$) \cdot Y_{RA}(\$)}{Y_{RC}(\$) + \frac{1}{2}Y_{RB}(\$)} \right) - V_1(\$) \cdot Y_{RA}(\$)$$

$$\frac{V_2(\$)}{V_1(\$)} = \frac{Y_{RC}(\$) \cdot \cancel{Y_{RB}(\$)} \cdot 1}{Y_{RC}(\$) + \frac{1}{2}Y_{RB}(\$) \cdot \cancel{Y_{RB}(\$)}} + \frac{Y_{RC}(\$) \cdot Y_{RA}(\$) \cdot 1}{Y_{RC}(\$) + \frac{1}{2}Y_{RB}(\$) \cdot Y_{RA}(\$)} - \frac{Y_{RA}(\$)}{Y_{RB}(\$)}$$

$$\frac{V_2(\$)}{V_1(\$)} = \frac{Y_{RC}(\$)}{Y_{RC}(\$) + \frac{1}{2}Y_{RB}(\$)} \left(1 + \frac{Y_{RA}(\$)}{Y_{RB}(\$)} \right) - \frac{Y_{RA}(\$)}{Y_{RB}(\$)}$$

$$Y_{RC}(\$) = \frac{1}{\frac{1}{\$C}} = \frac{1}{n + \frac{1}{\$C}} = \frac{\$C}{\$Cn + 1}$$

$$Y_{RB}(\$) = \frac{1}{\frac{1}{\$C}} = \frac{1}{\frac{1}{\$C} + \frac{1}{\$C}} = \frac{1}{\frac{2}{\$C}} = \frac{\$C}{2}$$

$$Y_{RA}(\$) = \frac{1}{nA}, \quad Y_{RB}(\$) = \frac{1}{nB}$$

$$\frac{Y_{RC}(\$)}{Y_{RC}(\$) + \frac{1}{2}Y_{RB}(\$)} = \frac{\frac{\$C}{\$Cn + 1}}{\frac{\$C}{\$Cn + 1} + \frac{\$C}{2n}} = \frac{\$C}{(\$Cn + 1) \left[\frac{\$C}{\$Cn + 1} + \frac{\$Cn + 1}{2n} \right]}$$

$$= \frac{\$C \cdot \frac{2n}{\$Cn + 1}}{\$C + \frac{(\$Cn + 1)^2}{2n}} = \frac{\$Cn}{\$Cn + \frac{(\$Cn + 1)^2}{2n}} = \frac{\$Cn}{\$Cn + \$^2 C^2 n^2 + 2\$Cn + 1}$$

$$= \frac{\$Cn}{\$^2 C^2 n^2 + 3\$Cn + 1} \cdot \frac{1/(Cn)^2}{1/(Cn)^2} = \frac{\$ / Cn}{\$^2 + 3\$ \cdot \frac{1}{Cn} + \frac{1}{(Cn)^2}} = \frac{Y_{RC}(\$)}{Y_{RC}(\$) + \frac{1}{2}Y_{RB}(\$)}$$

$$\frac{Y_{RA}(\$)}{Y_{RB}(\$)} = \frac{1/nA}{1/nB} = \frac{nB}{nA}$$

$$H(\$) = \frac{\$ / c.n}{\$^2 + 3\$ \frac{1}{c.n} + \frac{1}{(c.n)^2}} \left(1 + \frac{n.B}{n.A} \right) - \frac{n.B}{n.A} \quad (4)$$

$$H(\$) = \frac{\frac{\$ \cdot n.A}{c.n} \left(1 + \frac{n.B}{n.A} \right) - n.B \cdot \left(\$^2 + \$ \cdot \frac{3}{c.n} + \frac{1}{(c.n)^2} \right)}{\left(\$^2 + \$ \cdot \frac{3}{c.n} + \frac{1}{(c.n)^2} \right) \cdot n.A}$$

$$H(\$) = \frac{\$ \cdot \frac{n.A}{c.n} + \frac{\$ \cdot n.B}{c.n} - \$^2 n.B - \$ \cdot \frac{3 n.B}{c.n} - \frac{n.B}{(c.n)^2}}{\$^2 n.A + \$ \cdot \frac{3 n.A}{c.n} + \frac{n.A}{(c.n)^2}}$$

$$H(\$) = \frac{-\$^2 n.B - \$ \cdot \frac{2 n.B}{c.n} + \$ \cdot \frac{n.A}{c.n} - \frac{n.B}{(c.n)^2}}{\$^2 n.A + \$ \cdot \frac{3 n.A}{c.n} + \frac{n.A}{(c.n)^2}}$$

→ Transparencia, aspecto general

• Ahora aplica la relación $\frac{n.A}{n.B} = 5 \Rightarrow \frac{n.B}{n.A} = \frac{1}{5}$

$$\Rightarrow \text{Retomando (4)} \Rightarrow H(\$) = \frac{\frac{\$}{c.n}}{\$^2 + 3\$ \frac{1}{c.n} + \frac{1}{(c.n)^2}} \left(1 + \frac{1}{5} \right) - \frac{1}{5}$$

$$H(\$) = \frac{\frac{\$}{c.n} \cdot \frac{6}{5} \cdot 5 - \left(\$^2 + 3\$ \frac{1}{c.n} + \frac{1}{(c.n)^2} \right)}{\left(\$^2 + 3\$ \frac{1}{c.n} + \frac{1}{(c.n)^2} \right) \cdot 5}$$

$$H(\$) = \frac{-\$^2 - 3\$ \frac{1}{c.n} + 6\$ - \frac{1}{(c.n)^2}}{\$^2 + 3\$ \frac{1}{c.n} + \frac{1}{(c.n)^2}} \cdot \frac{1}{5} \quad / \quad K = \frac{1}{5}$$

$$H(\$) = \frac{-\$^2 + 3\$ \frac{1}{c.n} - \frac{1}{(c.n)^2}}{\$^2 + 3\$ \frac{1}{c.n} + \frac{1}{(c.n)^2}} \cdot \frac{1}{5} \quad \rightarrow \text{con } \frac{n.A}{n.B} = 5$$


Buses el módulo

$$S = 5\omega \Rightarrow H(5\omega) = \frac{+ (5\omega)^2 - 3 \cdot \frac{5\omega}{c \cdot n} + \frac{1}{(c \cdot n)^2}}{(5\omega)^2 + 3 \cdot \frac{5\omega}{c \cdot n} + \frac{1}{(c \cdot n)^2}} \cdot \frac{1 \cdot (-1)}{5}$$

$$H(5\omega) = \frac{-\omega^2 + 5 \cdot \frac{3\omega}{c \cdot n} + \frac{1}{(c \cdot n)^2}}{-\omega^2 + 5 \cdot \frac{3\omega}{c \cdot n} + \frac{1}{(c \cdot n)^2}} \cdot \frac{1}{5}$$

$$|H(5\omega)| = \frac{1}{5} \frac{\sqrt{\left(+\frac{1}{(c \cdot n)^2} - \omega^2\right)^2 + \left(-\frac{3\omega}{c \cdot n}\right)^2}}{\sqrt{\left(+\frac{1}{(c \cdot n)^2} - \omega^2\right)^2 + \left(\frac{3\omega}{c \cdot n}\right)^2}} = \frac{1}{5} = |H(5\omega)|$$

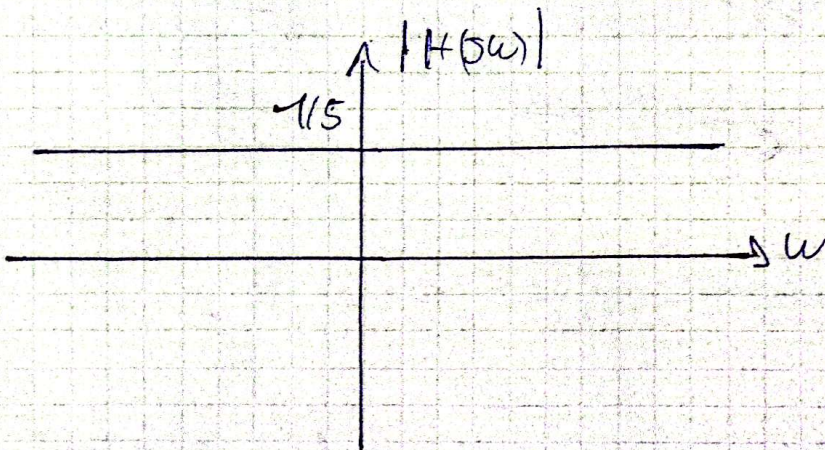• Por lo tanto el módulo es $\frac{1}{5}$



Buses la fase:

$$\phi_H(\omega) = \arctg\left(\frac{\text{Im}\{ \text{Num } H(5\omega) \}}{\text{Re}\{ \text{Num } H(5\omega) \}}\right) - \arctg\left(\frac{\text{Im}\{ \text{Den } H(5\omega) \}}{\text{Re}\{ \text{Den } H(5\omega) \}}\right)$$


$$\phi_H(\omega) = \arctg\left(\frac{-\frac{3\omega}{c \cdot n}}{\frac{1}{(c \cdot n)^2} - \omega^2}\right) - \arctg\left(\frac{\frac{3\omega}{c \cdot n}}{\frac{1}{(c \cdot n)^2} - \omega^2}\right)$$

$$\phi_H(\omega) = -\arctg\left(\frac{\frac{3\omega}{c \cdot n}}{\frac{1}{(c \cdot n)^2} - \omega^2}\right) - \arctg\left(\frac{-\frac{3\omega}{c \cdot n}}{\frac{1}{(c \cdot n)^2} - \omega^2}\right)$$

$$\phi_H(\omega) = -2 \arctg\left(\frac{\frac{3\omega}{c \cdot n}}{\frac{1}{(c \cdot n)^2} - \omega^2}\right)$$

$$\varphi_H(\omega) = -2 \arctg \left(\frac{\frac{3\omega}{c \cdot R}}{\frac{1}{(c \cdot R)^2} - \omega^2} \right) = -2 \arctg \left(\frac{3\omega}{-\omega^2 c R + 1} \right)$$

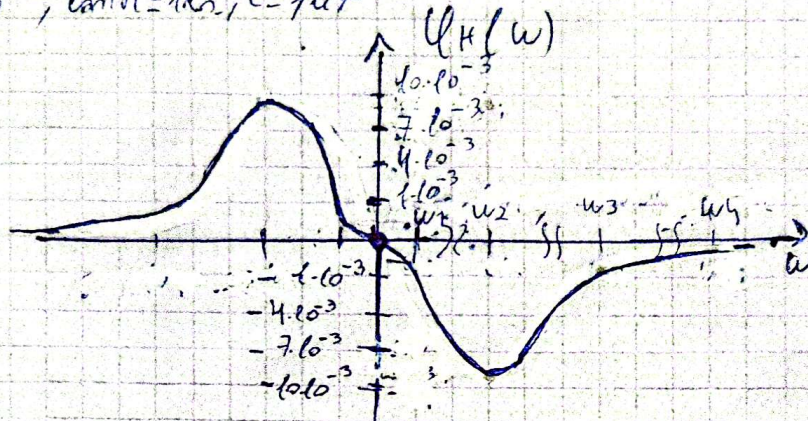$c \cdot R = 10^{-3}$, $\tan R = 1 \text{ K}\Omega$, $c = 1 \mu\text{F}$



- $\omega = 0 \Rightarrow \varphi_H(0) = 0$
- $\omega \rightarrow +\infty \Rightarrow \varphi_H(\omega) \rightarrow 0$
- $\omega \rightarrow -\infty \Rightarrow \varphi_H(\omega) \rightarrow 0$

- $f_1 = 10 \text{ KHz} \Rightarrow \omega_1 = 2\pi \cdot 10^4 \text{ rad/s}$
- $f_2 = 100 \text{ KHz} \Rightarrow \omega_2 = 2\pi \cdot 10^5 \text{ rad/s}$
- $f_3 = 1 \text{ MHz} \Rightarrow \omega_3 = 2\pi \cdot 10^6 \text{ rad/s}$
- $f_4 = 10 \text{ MHz} \Rightarrow \omega_4 = 2\pi \cdot 10^7 \text{ rad/s}$

$\varphi_H(\omega)$ rad	f
0	0
$\approx \pm 0.37 \cdot 10^{-3}$	$\pm 10 \text{ KHz}$
$\approx \pm 0.6 \cdot 10^{-3}$	$\pm 100 \text{ KHz}$
$\approx \pm 0.95 \cdot 10^{-3}$	$\pm 1 \text{ MHz}$
$\approx \pm 0.095 \cdot 10^{-3}$	$\pm 10 \text{ MHz}$


Diagrama de polos y ceros

$$H(s) = \frac{-s^2 + 3 \frac{s}{c \cdot R} - \frac{1}{(c \cdot R)^2}}{s^2 + 3 \frac{s}{c \cdot R} + \frac{1}{(c \cdot R)^2}} \cdot \frac{1}{5}$$

Si $c \cdot R = 10^{-3}$ $\tan R = 1 \text{ K}\Omega$, $c = 1 \mu\text{F}$

$$H(s) = \frac{(s - 2618.03) \cdot (s - 381.966)}{(s + 2618.03) \cdot (s + 381.96)} \cdot \frac{1}{5}$$

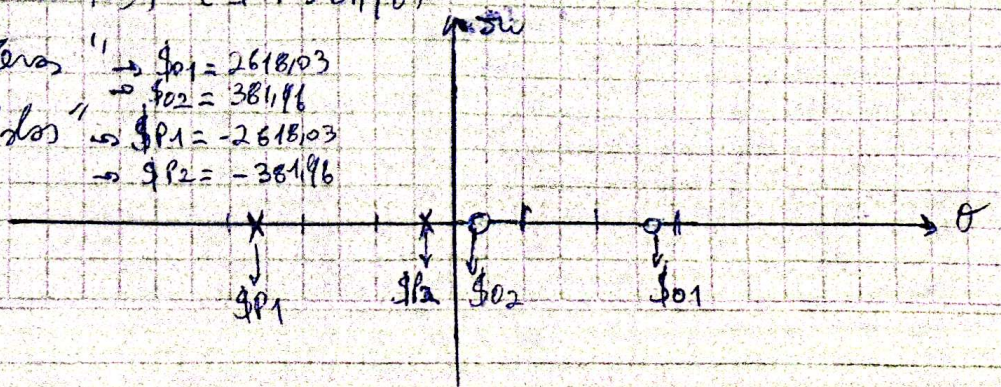- Numerador de "ceros" $\rightarrow s_{01} = 2618.03$
 $\rightarrow s_{02} = 381.96$
- Denominador de "polos" $\rightarrow s_{p1} = -2618.03$
 $\rightarrow s_{p2} = -381.96$



NOTA